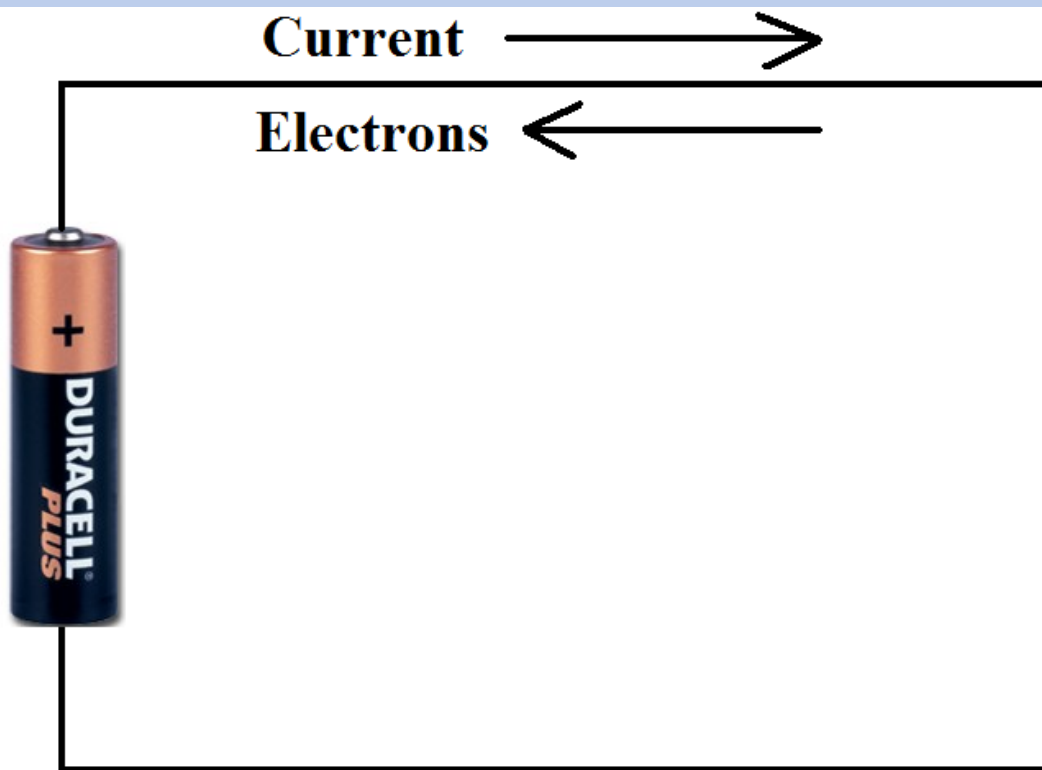


Themed: 06-01

Basic circuit example, schematic, Resistors, batteries
& symbols/units, series resistors, current, voltage,
Ohm's law

Basic circuit example


- Voltage source shorted with a wire
- Current: Flow of positive charge (opposite of what's really flowing (electrons))
- Electrical conductors (metals) have loosely bound valence electrons, which move charge freely



When we say charge flows from one point to another, we really mean the anti-flow of electrons, don't let this confuse you! (keep in the back of your mind)

Basic circuit example - Bulb

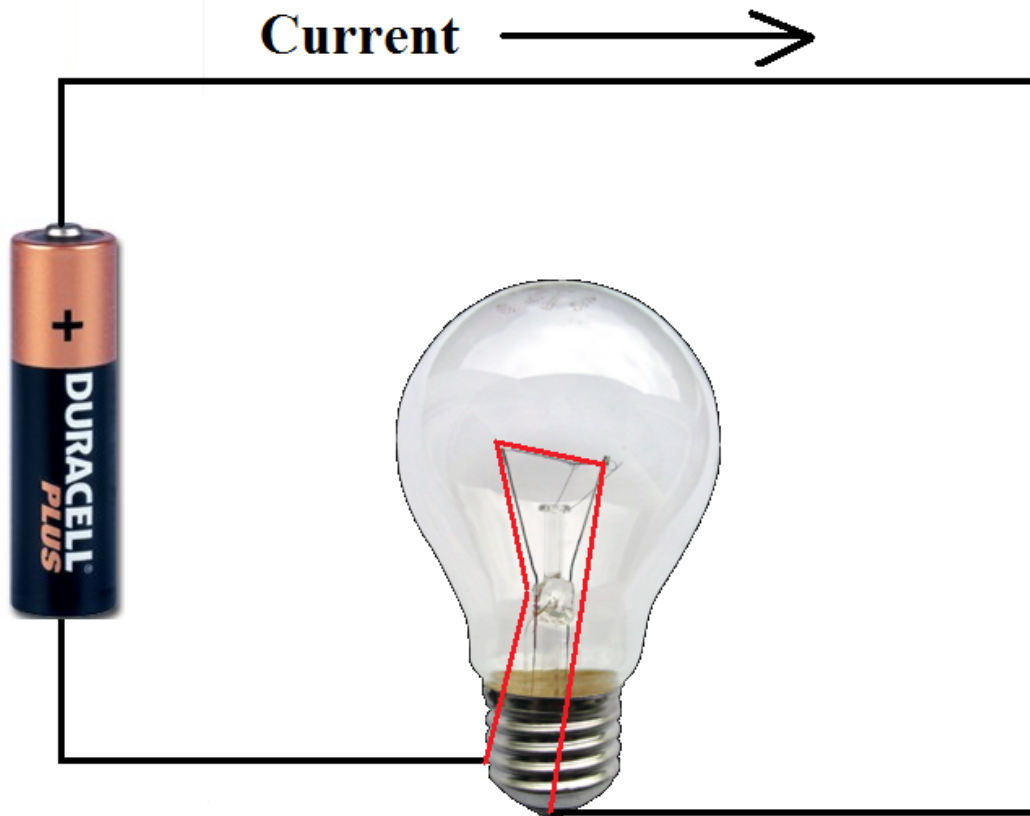
- Voltage source pushes electrons through resistance
- Bulb is a resistor you'll use for six days.
- Understand charge flows through bulb going in the bottom and out the side



Without resistance, electrons flow too fast and wire heats up a “short circuit” (previous picture of “simplest circuit”)

Basic circuit example - Filament


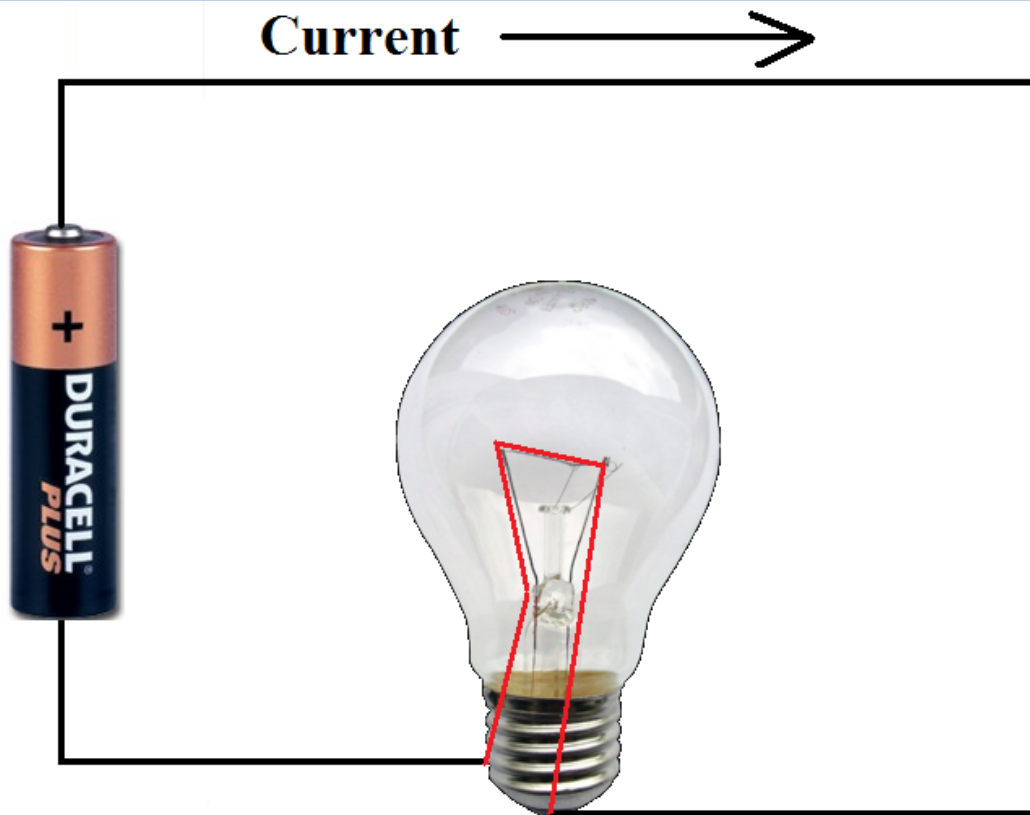
- Thin wire in bulb is called the filament
- Wire bulbs are incandescent, meaning they are so hot they glow – most energy is wasted in heat



- Thick filaments are bright (lots of room for many electrons)
- Thin filaments are dim (narrow, few electrons can flow)


Schematic

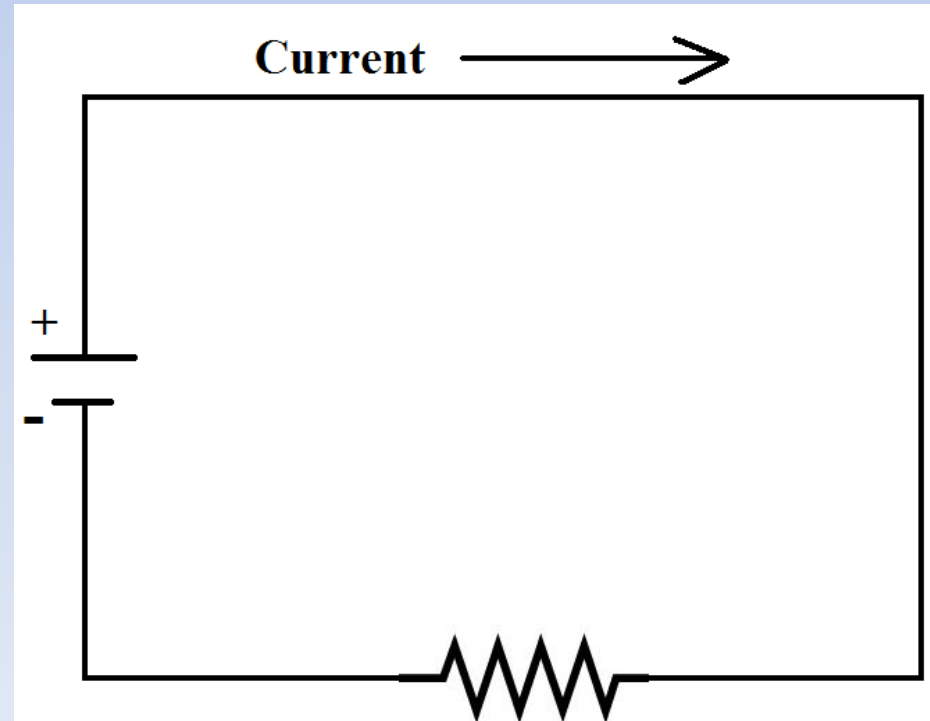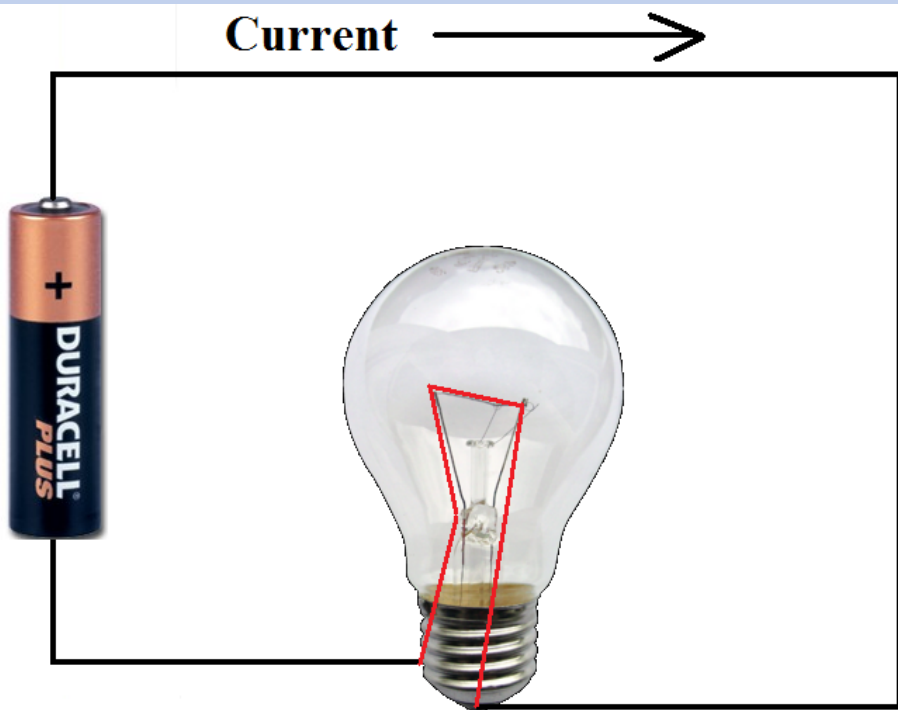- Rather than drawing realistic-looking bulbs and batteries, we use symbols
- Batteries, or voltage sources have a wide positive and a narrow negative
- Resistors have a sawtooth symbol, sometimes put a circle around resistor symbol to symbolize a bulb



Resistors, batteries & symbols/units

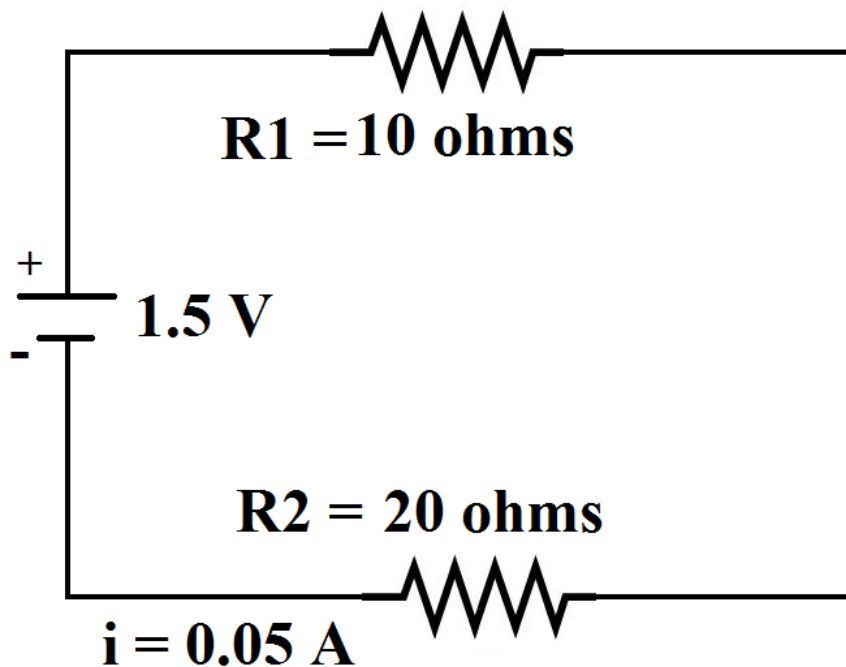- Resistors resist flow of charge
- Resistance (R) is measured in ohms (Ω)
- More ohms = more resistance to flow of charge
- Battery “push” voltage (V) measured in volts (V)
- Current (i) measure in amps (A)




- 1 amp = 1 coulomb of charge flowing by any particular point in a wire each second

- In calculations, Copper wire is usually assumed to have no resistance

Series resistors– shopping analogy

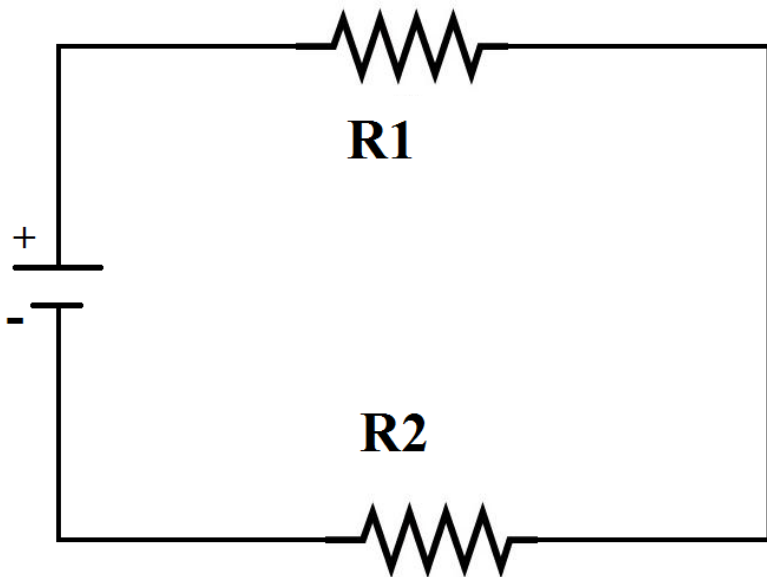
- Imagine you're doing holiday shopping
- First: Wait in check out line
- Second: Wait in gift box line
- Do two consecutive lines speed flow of shoppers?
- Two consecutive resistors are in “series”



- Resistors in series have more resistance
- We'll learn the math for series and parallel resistors later

What is current?

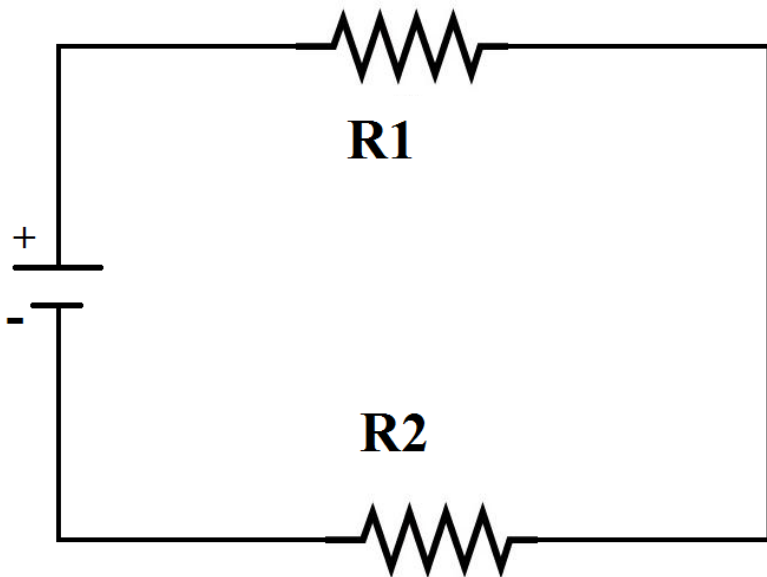
- Conventional Current is the flow of positive charge
- Electrons flow the opposite way
- Measure in Amps, short for amperes
- Symbol for current is I
- $I = Q/t$



- What direction does current flow?
- What direction do electrons flow?

What is voltage?

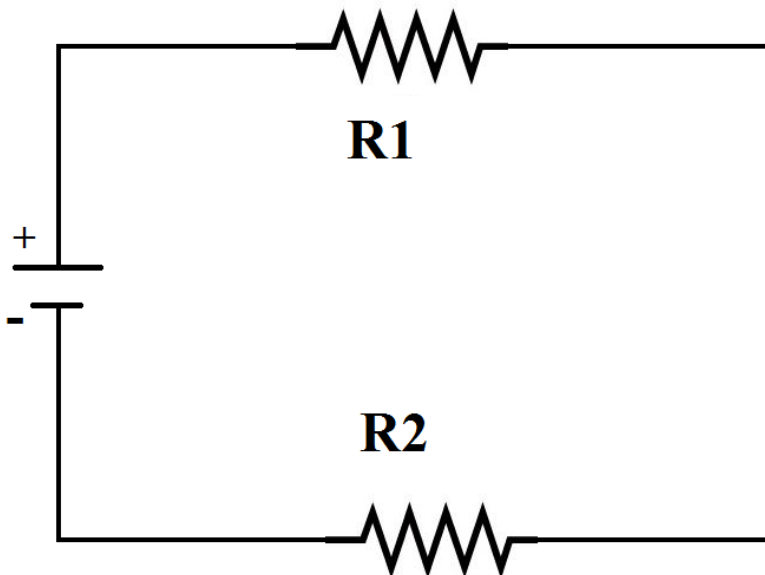- Voltage is the push of charge toward lower voltage
- Think of +/- as elevation, charge goes downhill
- AKA: emf (electromotive force)
- Schematic shows wide end as +, narrow as –
- Voltage drops across resistance ONLY
- In calculations, we assume wire has zero resistance



- Which has higher voltage, left of R1 or right of R1?
- Which has higher voltage, left of R2 or right of R2?

Ohm's law

- The relationship between voltage, current and resistance is called Ohm's law and is the cornerstone of current electricity:

$\Delta V = iR$ (voltage drop = current flow x resistance to current flow)

Example: how much current flows when a 12 volt battery is wired to a 4 ohm resistor?
(draw a schematic & solve)


(3A)

Themed: 06-02

Parallel resistors, Cost of electricity, Wire
resistance/drift velocity


Parallel resistors

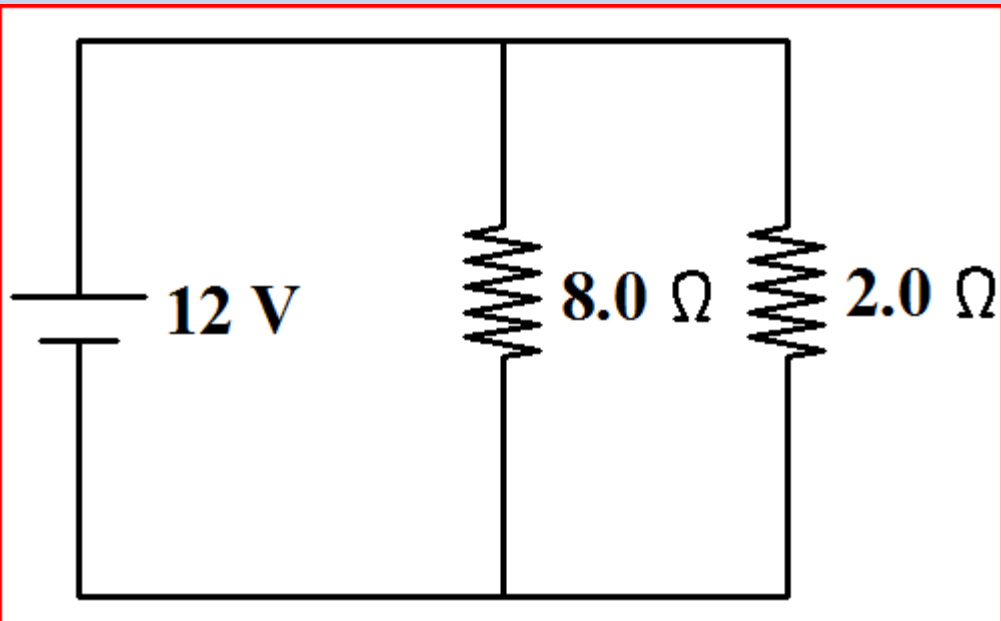- You leave your car to go shopping
- To return to your car, must check out
- One cashier is really slow; the other is fast
- Which has the most resistance to the flow of shoppers?
 - Would it speed things up if there were only one cashier?
 - Does opening another traffic lane help?
 - Do you see how parallel is a fork in the road? Would a third parallel resistor help?



Parallel resistors – overall resistance

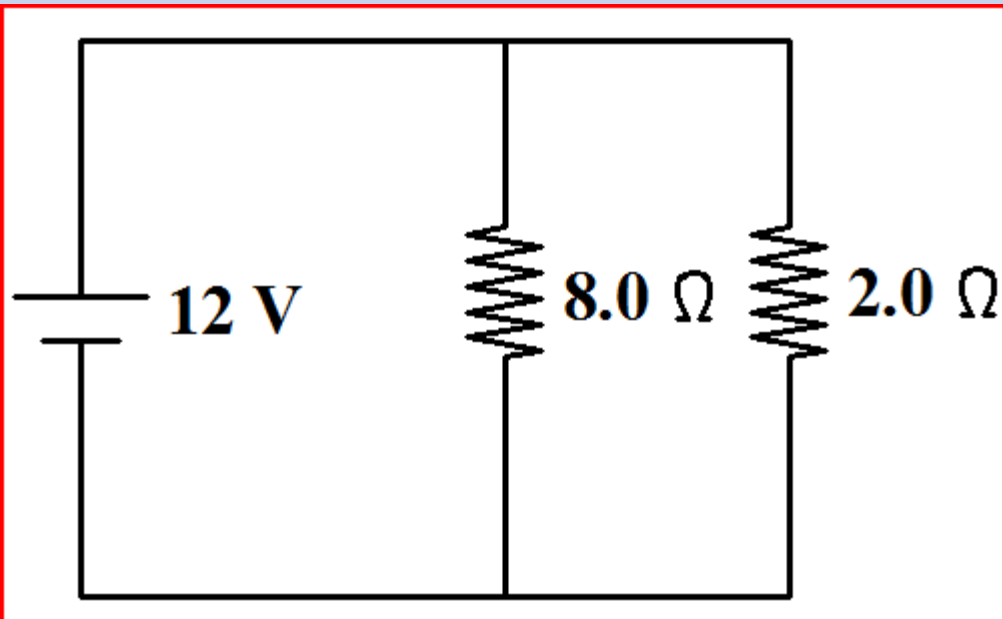- What can you say about the overall resistance below in ohms? (>8 , >2 , <2 , between 2 and 8)?
- There's math to figure this out, we'll do that later



Cost of electricity

- This is my ComEd bill from Fall 2013
- Using 705 kw-hrs cost me \$85.25
- To nearest penny this is 12 cents/kw-hr (you'll memorize this)
- 5 yrs ago we used 10 cents!

Page 1 of 2

Account Number		Bill Summary	
Name		Previous Balance	\$136.17
Service Location		Total Payments - Thank You	\$136.17
Phone Number		Amount Due on October 25, 2013	\$85.25

Issue Date October 3, 2013 **Late payment charges will continue until bill is paid.**

Meter Information								
Read Date	Meter Number	Load Type	Reading Type	Previous	Meter Reading Present	Difference	Multiplier X	Usage
10/1	093666741	General Service	Total kWh	94611 Actual	95316 Estimate	705	1	705

Service from 9/5/2013 to 10/1/2013 - 26 Days Retail Delivery Service - Res Single

Electricity Supply Services - ResCom		\$49.28
RES CHARGES	705 kWh X 0.06990	49.28
ResCom 1-855-572-8374		
Please refer to your supplier contract for details.		
Delivery Services - ComEd		\$30.16
Customer Charge		12.79
Standard Metering Charge		2.86
Distribution Facilities Charge	705 kWh X	0.01937
IL Electricity Distribution Charge	705 kWh X	0.00120
		0.85
Taxes and Other		\$5.81
Environmental Cost Recovery Adj	705 kWh X	0.00039
Energy Efficiency Programs	705 kWh X	0.00186
Franchise Cost	\$29.59 X	3.71200%
State Tax		2.33
Municipal Tax		0.80
Total Current Charges		\$85.25









Cost of electricity

Equations to use:

- $P = iV$ (power in watts = current in amps x voltage)
- $P = E/t$ (power = energy/time)
- $E = P t$ (same equation above, solved for energy)
- **Do you pay for power or energy? How much does it cost to run a 100 W light bulb? What's missing (or Watt's missing!)?**
- Use $E = P t$ where E is kilowatt-hours (convert time to hours and power to kilowatts)
- Example: How much does it cost to run a 40 watt night light 12 hrs every night for 365 days?
- Example 2: To light a tennis court indoors at my club takes eight bright lights. I think they're 1000 watt lights. Assuming that's right and assuming my club gets an industrial rate half of mine, how much does it cost them to light up a tennis court for an hour?

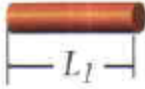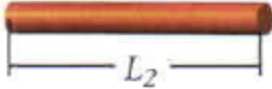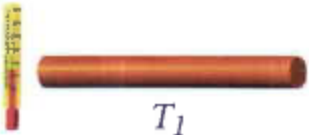Drift Velocity & Factors affecting wire resistance

- Drift velocity: Average speed of electrons in circuit...Electrons move slow, current sets up at light speed
- Yes, assume resistance for calculations, but.....
- Know what affect wire resistance
- Harder to move charge = more resistance

Factor	Less resistance	Greater resistance
Length		
Cross-sectional area		
Material	 Copper	 Iron
Temperature		


- Has farther to go
- Has fewer electrons to help move charge
- Material property
- Hotter = more atomic vibration = more R

Themed: 06-03

Solving Simple Circuits Mathematically, Wire paths make voltages same!, examples, Circuit strategies, Finding power & cost


Solving Simple Circuits Mathematically

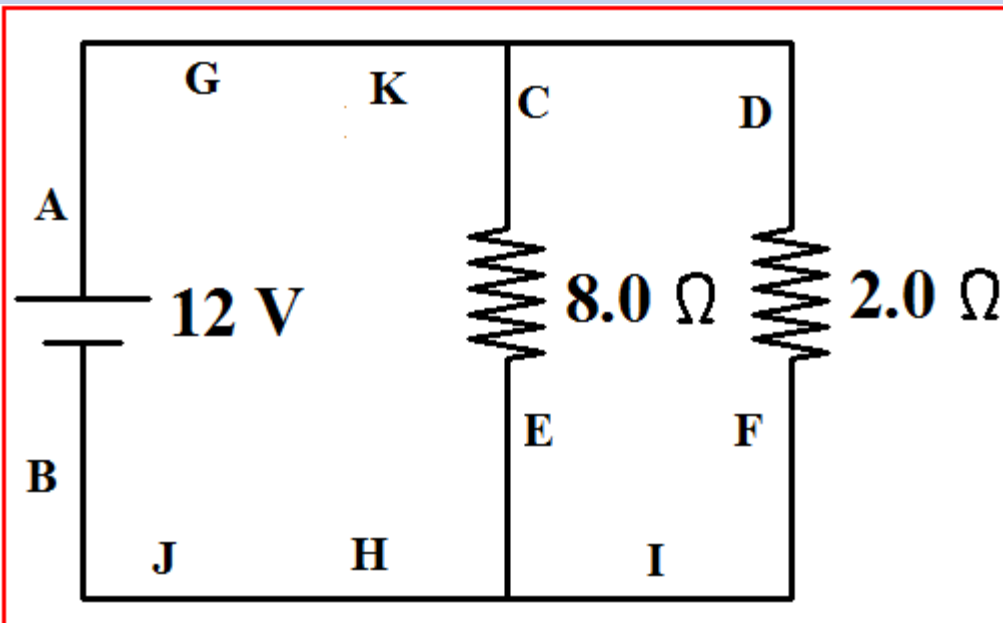- Combine resistors & solve via Ohm's law
 - Realize voltage drops only take place over resistors
 - Combine in series: $R_e = R_1 + R_2$
 - Combine in parallel: Parallel $1/R_e = 1/R_1 + 1/R_2$
- Which pts have 12 V? 0 V?
 - How much current goes
 - Through 8Ω resistor?
 - Through 2Ω resistor?
 - In/out of battery?
 - What's R_e for this circuit?
 - How much current does that R_e predict?




Wire paths make voltages same!

- Remember: For any calculation, assume no resistance in copper wires
- $V = iR$ says that: No voltage drop occurs over wire
- Voltage only drops across resistors!
- Which voltages are the same?

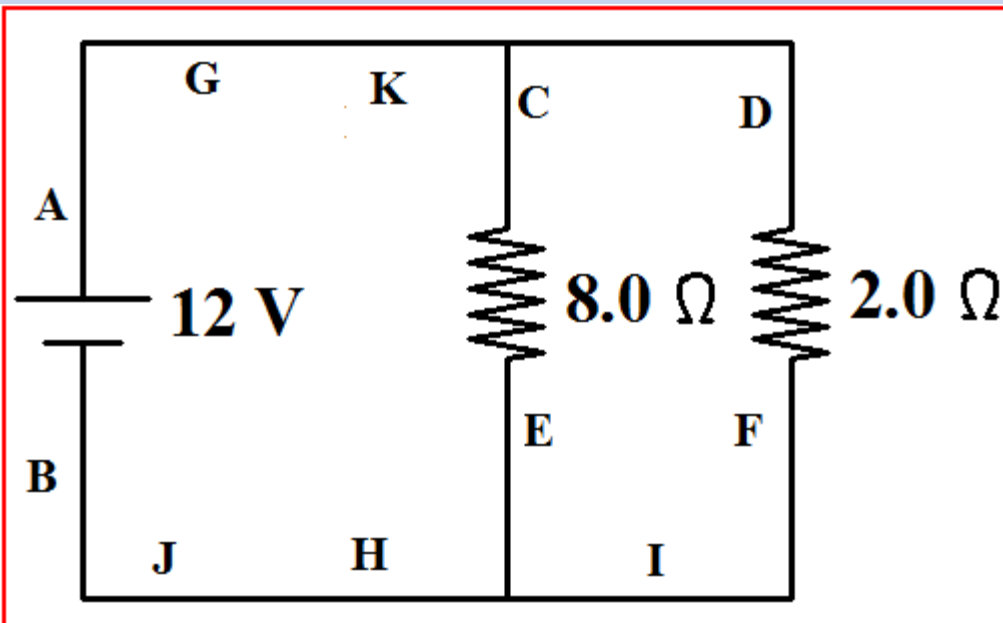


Example 1: Resistors in parallel

- Resistors in parallel have the same voltage drop across them
- What would be the equivalent resistance for this circuit?
- Now you can find the current entering/leaving battery

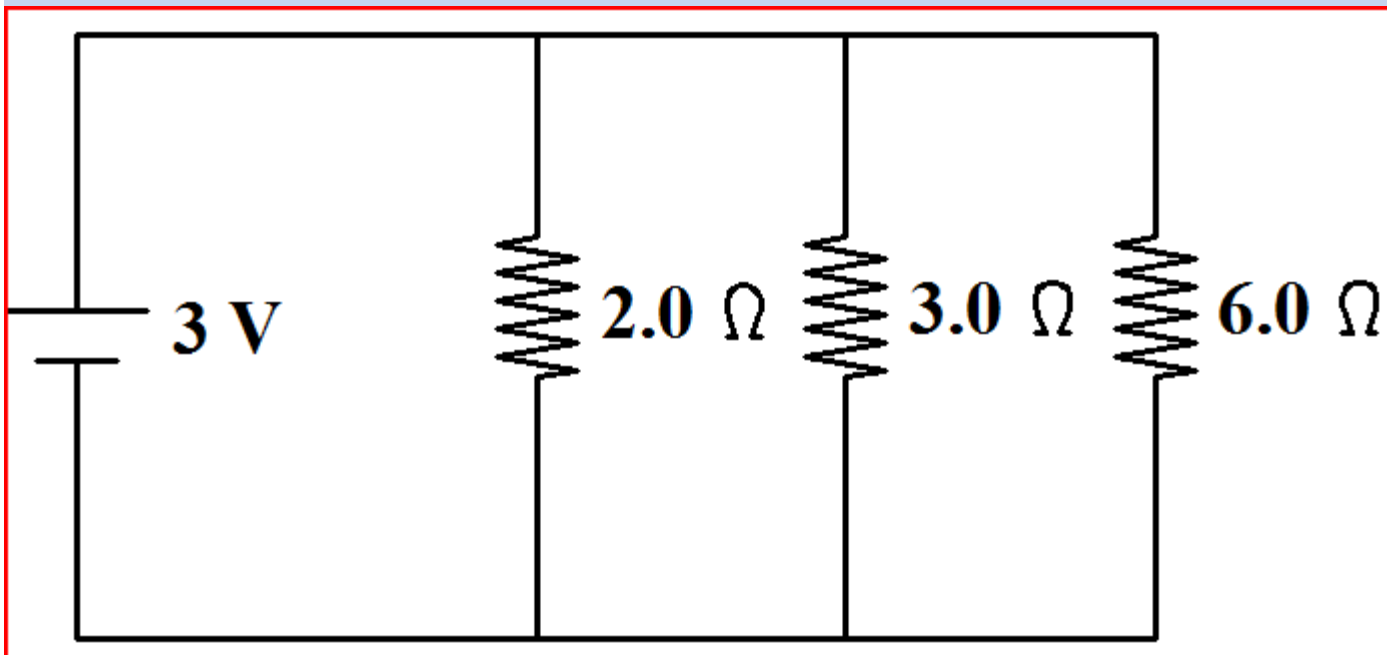


Example 2: Resistors in series

- Resistors in series have the same current passing through them
- Where could current possibly split off?
- What would be the equivalent resistance for this circuit?

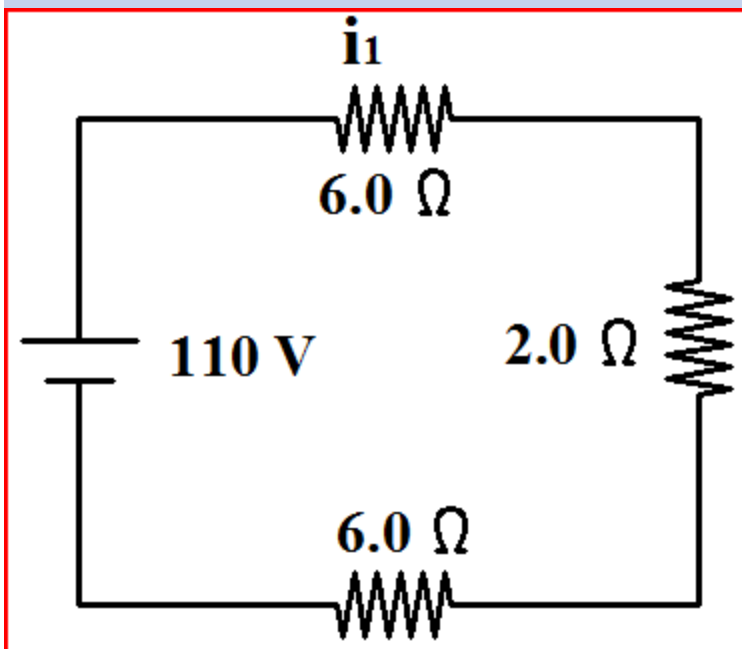

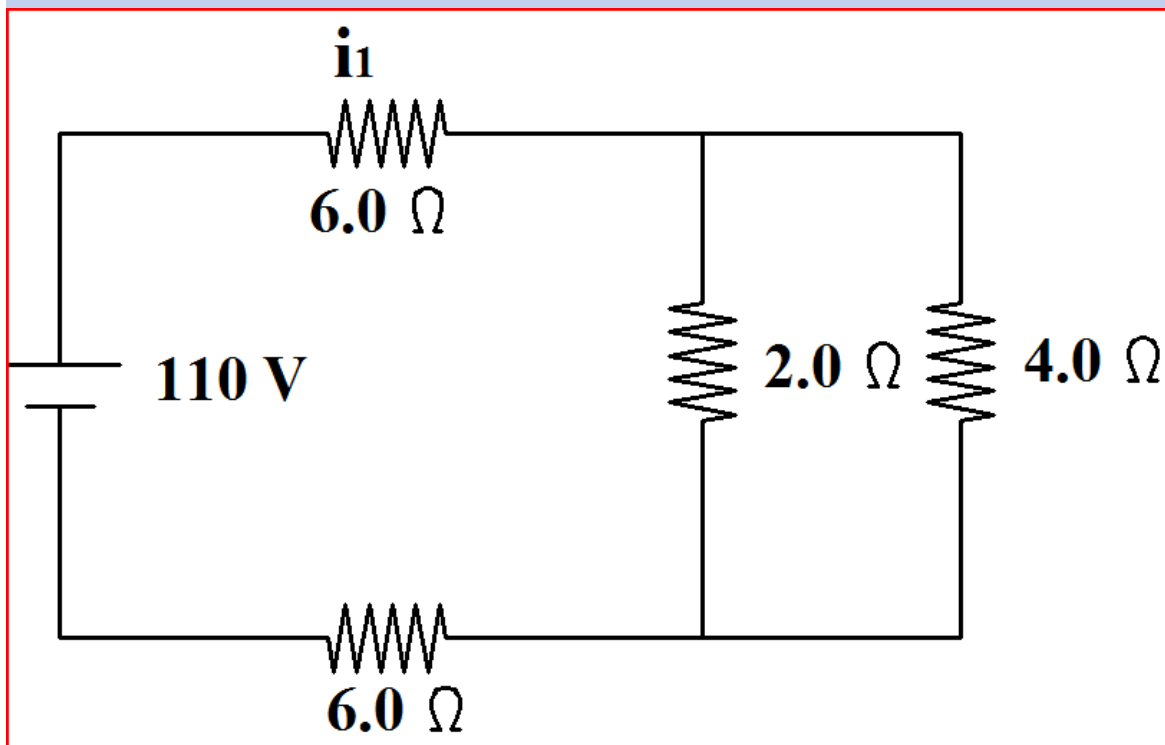Example 3: Mixed circuits

- How would you figure the equivalent resistance for this circuit?
- Two resistors in series: When current HAS to leave one and enter the next
- Two resistors in parallel: When they have the same entrance and exit voltages
- Do you see how neither the 2 or 4 ohm resistors are in series, but their equivalent is?



- Do it in two steps:
 - 1) find R_e for 2 and 4 ohm resistors
 - 2) add all three now in series

Themed: 06-04

Circuit board care, Multimeter: introduction, plug placement, dial setting, conductivity test, ammeter/voltmeter: circuit placement, examples

Circuit board care

- Note your board number (same each time)
- Always paper underneath
- Battery voltage (ALL alkaline batteries are 1.5V DC...know this!)
- Weak solders sometimes, treat carefully, especially bulbs – NEVER pick up by battery holder!
- NEVER twist or bend a resistor!
- Show bulb side and bottom

Multimeter – intro and plug placement

- Multimeter is 3-in-1 meter
 - Ohmmeter: measures resistance
 - Voltmeter: measures voltage drops (difference)
 - Ammeter: measures amps (current)



- Multimeter is a circuit itself, so must have a “return” lead – black lead into COM port
- Black port never changes
- Red port V Ω plug: Volt or ohmmeter
 - High resistance
- Red port 10A: ammeter
 - Low resistance

Multimeter – Dial Setting

- Multimeter has three dial settings:

1. Voltage (DC voltage..what we're using)
2. Amps (ammeter)
3. Ohms (ohmmeter)




- We won't use AC voltage region – this is for dangerous voltages we don't experiment with
- Top setting is OFF, leave here or battery drains
- Bottom setting is conductivity tester – sees two spots on board are SAME

Multimeter – Conductivity Tester

- Beeps when leads are placed on conductive path (dial is set at “6:00”, pointed downward)
- Useful for testing if spring points are electrically the same
- Useful to check for burnt out bulb, break in circuit (de-soldered piece, etc.)
- Try checking all your bulbs now
- Check battery voltages are at least 1.1 V (let me know if below 1.25 V)
- Do Multimeter lab (2 pages)

Ammeter/voltmeter: circuit placement

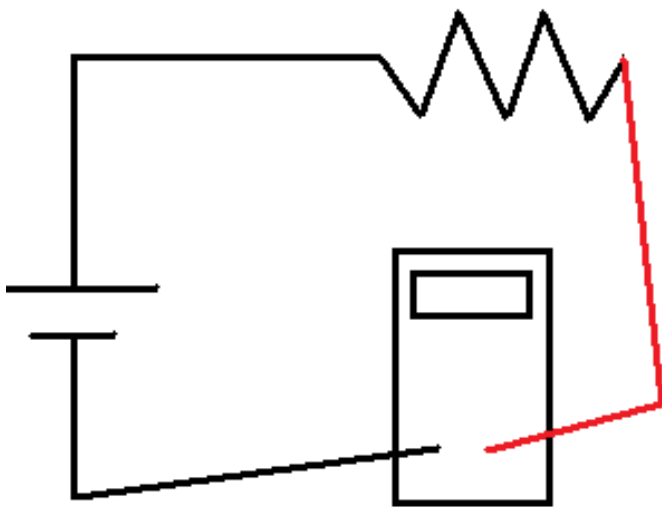
- Ammeter counts how many charges per second (this is what current is! – a charge CENSUS TAKER)
- All current must pass through ammeter for accurate count
- Ammeter can't have resistance, or would change circuit (would add resistance!)
- Ammeter must behave like wire – no resistance and be part of circuit (count all charges)



- Like always, red lead is on more positive side (though almost zero voltage drop)
- Reverse this & get negative current

Ammeter/voltmeter: circuit placement

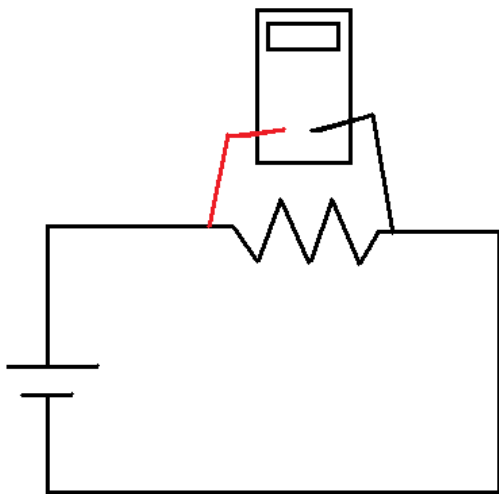- Voltmeter compares voltage in two locations and subtracts black value from red value
- Voltmeter is high resistance device (**otherwise would short circuit what it's measuring!**)
- Not counting charges (want tiny amt. of current)



- Resistance like voltage (compare entrance to exit, not counting number of charges)
- For SAME REASON, want device to have huge resistance
- BOTTOM LINE: These devices are placed in parallel (opposite of ammeter)

Multimeter – examples

- Set dial to max value you expect, if value too high, get error message (1 . ?) and not a real value
 - Plug AND dial in correct locations? Red lead in right place?
 - Example: Measure two batteries in series with setting of 2 and setting of 20...which works? Any batteries <1.1 V?



- Place a resistor on boardPLEASE DON'T TWIST!
- Find the resistance (dial and plug!)
- Connect via wire and measure current (dial and plug and part of circuit)

Board and make wires

- Every pair make 3 or 4 wires
- Make wires 9", strip ends enough to easily grasp
- Will help with robot project?

Themed: 06-05

Resistor codes, Schematics & equivalent equipment diagrams, Consequences of bulb changes

Resistor codes


- Resistor codes use three colored stripes
- Fourth stripe is quality control codes (for accuracy, not for determining resistor value)

Reading a resistor code

Finding how many ohms a resistor is

- First two stripes are first two digits
- Third stripe tells how many zeros go after second digit
- You won't have to memorize colors, just use them
- Try some examples.....

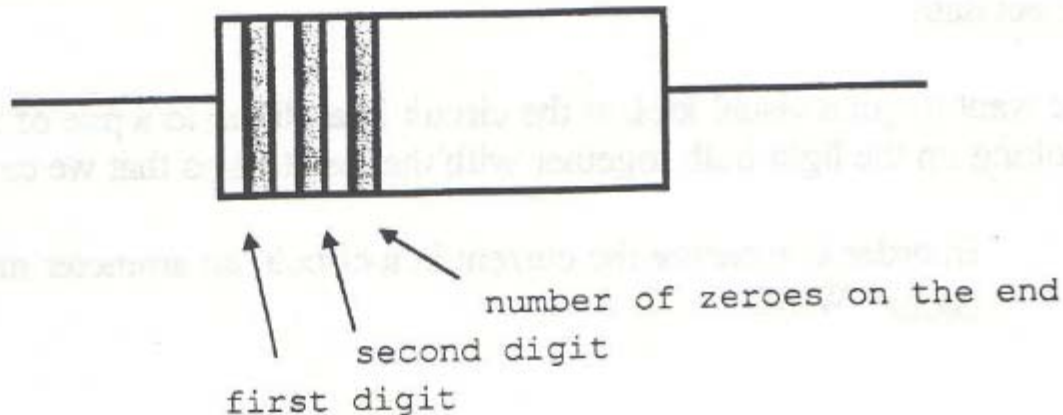0 = black
1 = brown
2 = red
3 = orange
4 = yellow
5 = green
6 = blue
7 = violet
8 = gray
9 = white




Reading a resistor code

Finding how many ohms a resistor is

- 10 ohms, 100 ohms, 1000 ohms
- 730 ohms, 73 ohms
- Orange, black, black
- Violet, yellow, yellow
- Brown, black, black
- Brown, brown, black
- More practice available in packet!

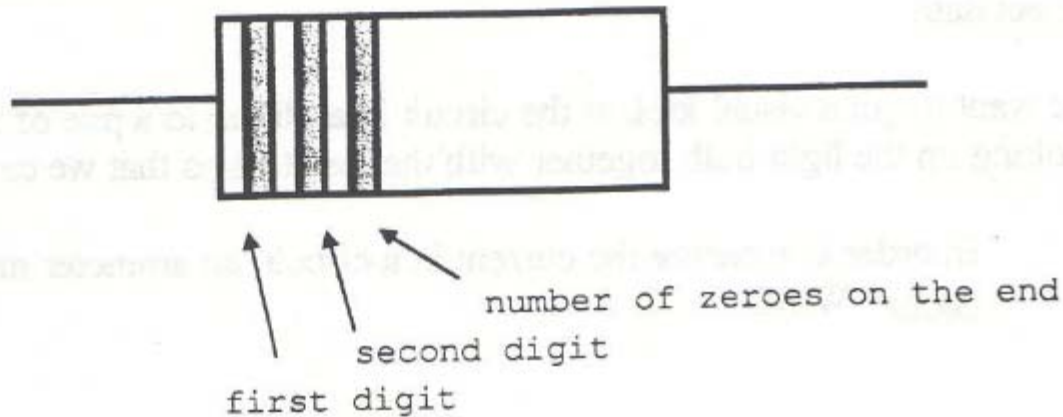
0 = black
1 = brown
2 = red
3 = orange
4 = yellow
5 = green
6 = blue
7 = violet
8 = gray
9 = white



Schematics & equivalent equipment diagrams


Color coding helps, use colored pencils if handy

- Schematic uses symbols (sawtooth for resistor, etc.)
- Equipment diagrams: practical translation of schematic onto real circuit board model
- Example: Ammeter measuring current through circuit with 1.5V and single 10 ohm resistor
- Can you follow color-coding of like-parts in schematic and equipment? See how red lead is in more positive place?
- Try it and see if current is like theory predicts! ($i = V/R$)
- Work on packets according to calendar

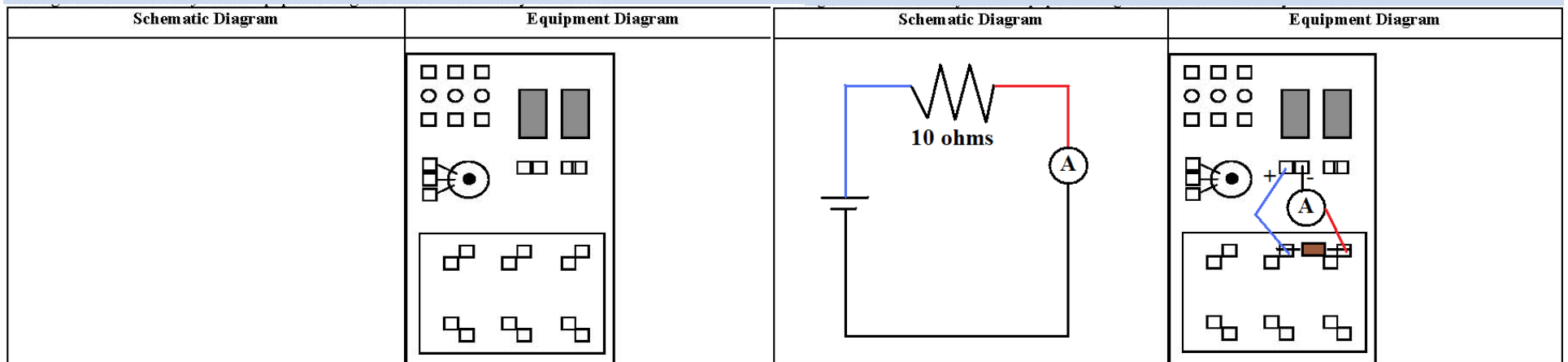



Consequences of bulb changes

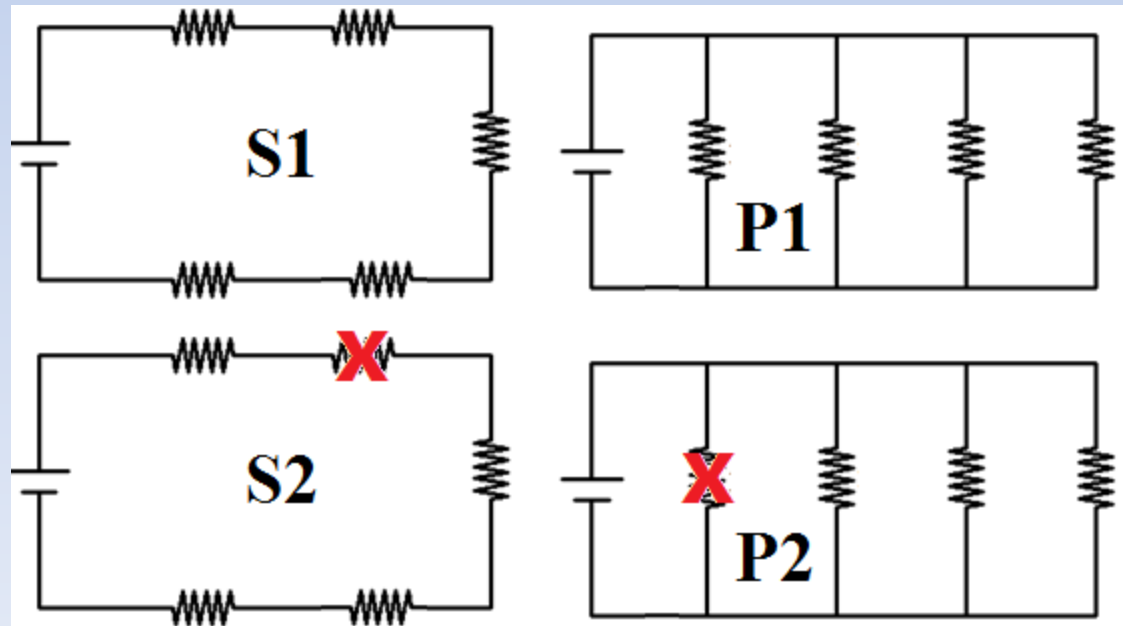- Series circuit: Bulb out = circuit open, no light!
- Parallel circuit: Bulb out = remaining bulbs still get same voltage, burn just as bright!
- Added bulbs: Series, less voltage per bulb – dimmer!
- Added bulbs: Parallel, same volts per bulb, same brightness



Consequences of bulb changes

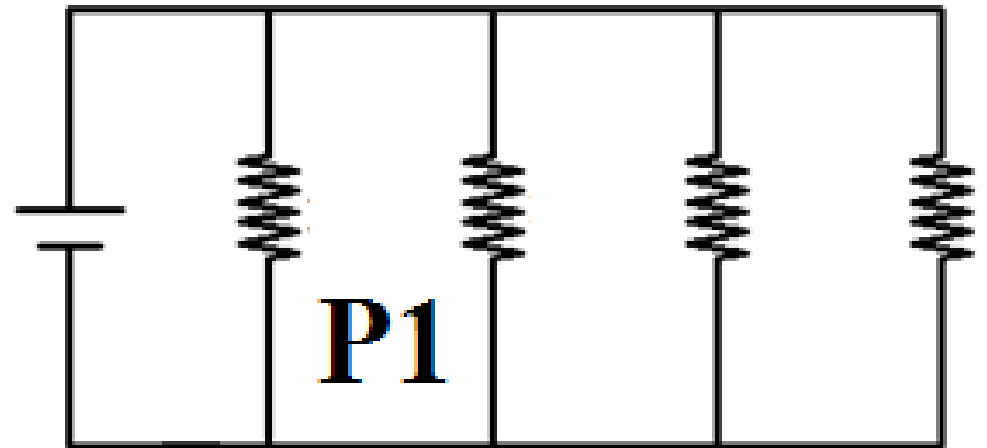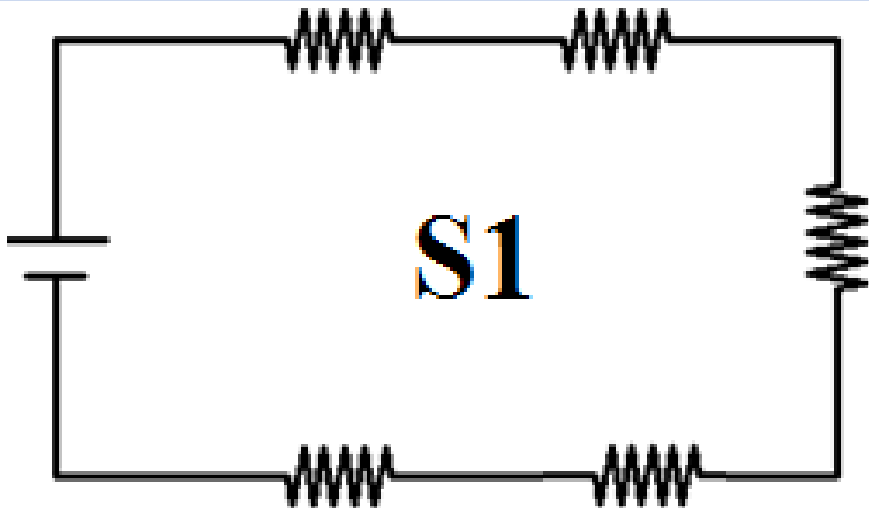- Power: more parallel resistors = less overall resistance = more current = more power
- Power: more series resistors = more overall resistance = less current = less power




Themed: 06-06

AC vs DC, Electricity kills, Circuit breakers/fuses

AC vs. DC

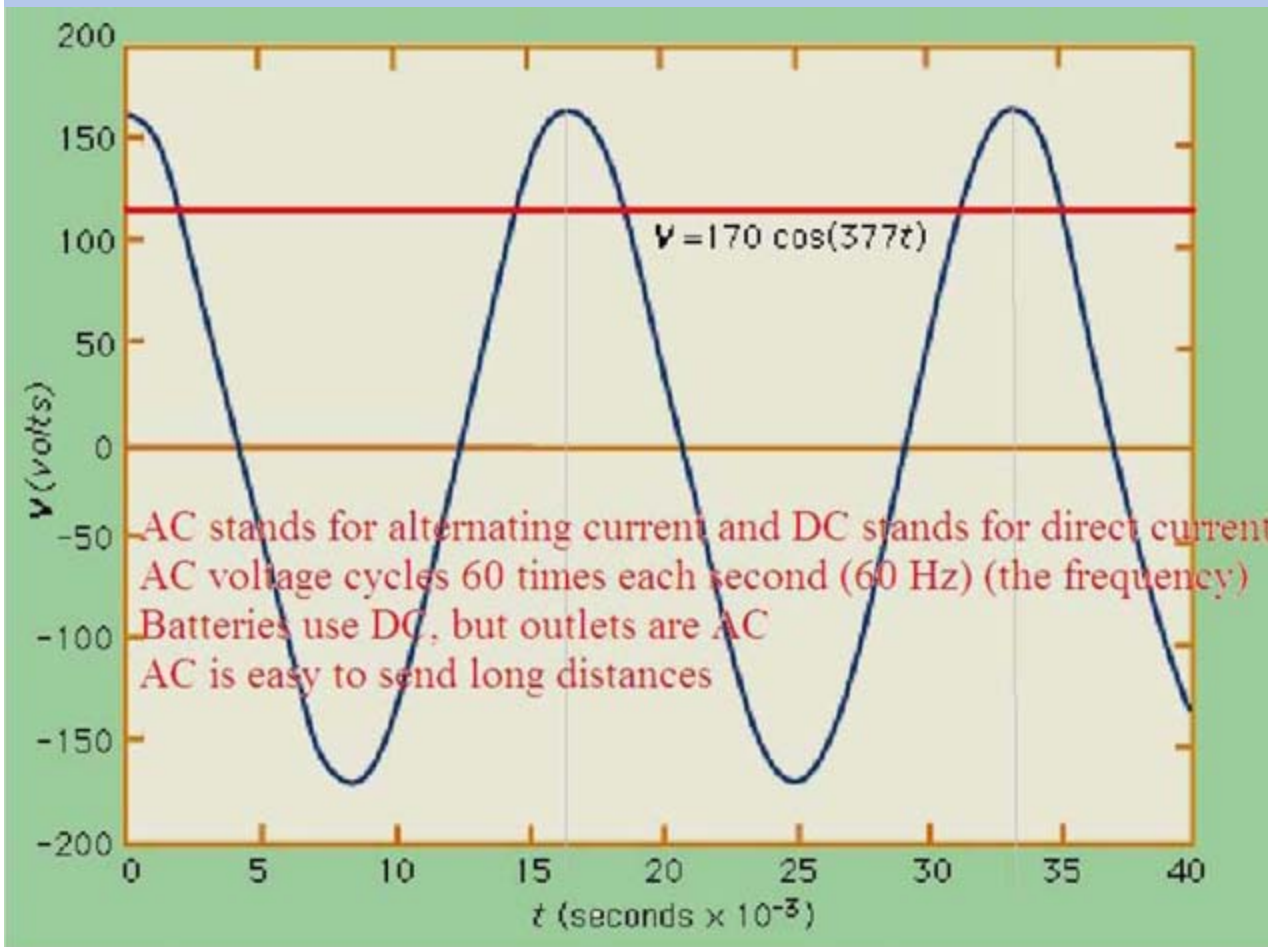
- AC stands for **A**lternating **C**urrent
- DC stands for **D**irect **C**urrent
- Tesla and Edison battled over which to use: Tesla won



- AC can go large distances without losing much energy; DC can't....this is why Tesla won!
- North American voltage is 120 V and frequency is 60 Hz (know this!)

AC vs. DC

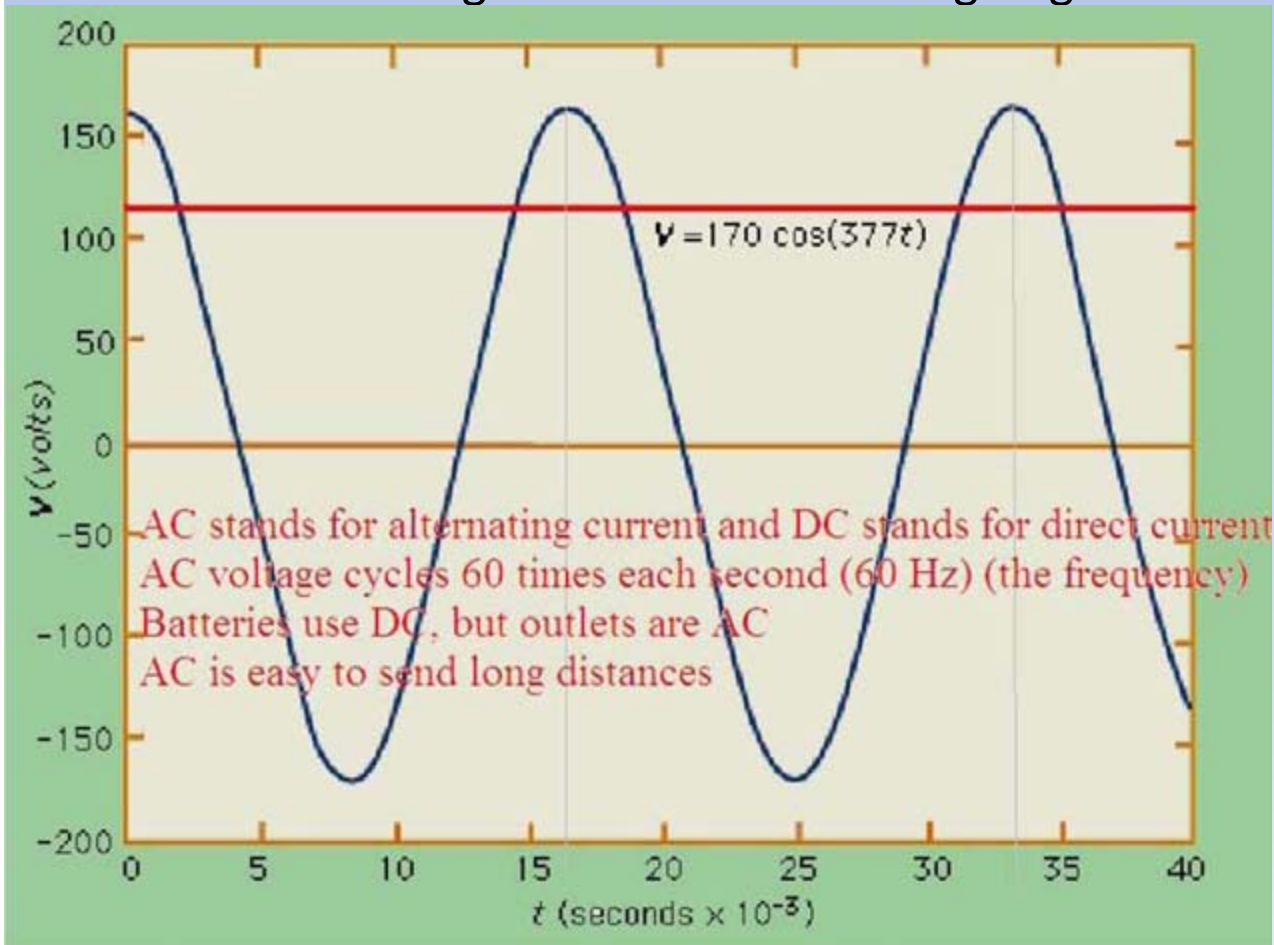- AC voltage varies continuously at 60 Hz
 - Push charges left at 170 volts, push charges right at 170 volts, repeat
 - Electrons don't move from power company to you – Power company only swishes them back and forth for you
 - Average magnitude of voltage is 120 volts
 - Bulb burn bright whether electrons go right or left



Electricity kills

- High voltage produces high current...but: Current kills, not voltage
- Static shocks have high voltage, but little current
- Human resistance varies by 100x depending on dry skin vs. wet/salty (sweating)
- Wounds have extremely low resistance (insulating skin is gone, leaving salt water body directly exposed)
- Left pocket rule (keep current from heart)

